

211: Computer Architecture Spring 2021

Assignment Project Exam Help
Instructor: Prof. David Menendez

Topics: <https://powcoder.com>

- Digital Logic
- Reading material available on Sakai

Add WeChat powcoder

Logic Design

Assignment Project Exam Help

How does your processor perform various operations?

<https://powcoder.com>

Add WeChat powcoder

Logic Gates

Transition from representing information to implementing them

Logic gates are simple digital circuits


- Take one or more binary inputs
- Produce a binary output
- Truth table: relationship between the input and the output

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Not Gate

 

Truth table

Assignment Project Exam Help

<https://powcoder.com>

Simplest Gate

In	Out
0	1
1	0

Add WeChat powcoder

AND Gate

Two inputs, One output


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Result is 1 only if both the inputs are 1.

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

 

AND

OR Gate

 

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.


NAND and NOR Gate

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

 

NOR

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

 

NAND

Beneath the Digital Abstraction

A digital system uses discrete values

- Represent it with continuous variables (eg, voltage), handle noise

Use transistors to implement logical functions: AND, OR, NOT

Digital symbols: **Assignment Project Exam Help**

- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V
 - from now on we'll use +2.9V

Transistor: Building Block of Computers

Microprocessors contain millions (billions) of transistors

- Intel Pentium 4 (2000): 48 million
- IBM PowerPC 750FX (2002): 38 million
- IBM/Apple Assignment Project Exam Help
PowerPC G5 (2003): 58 million

Logically, each transistor acts as a switch
<https://powcoder.com>

Combined to implement logic functions
Add WeChat powcoder

- AND, OR, NOT

Combined to build higher-level structures

- Adder, multiplexer, decoder, register, ...

Combined to build processor

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:



**To convert AND to OR
(or vice versa),
invert inputs and output.**

A	B	\overline{A}	\overline{B}	$A \cdot B$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	0	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	1	0

<https://powcoder.com>

Add WeChat powcoder

Generally, DeMorgan's Laws:

$$1. \overline{PQ} = \overline{P} + \overline{Q}$$

$$2. \overline{\overline{P} + \overline{Q}} = \overline{\overline{P}} \cdot \overline{\overline{Q}}$$

Same as A+B!

NAND and NOR Functional Completeness



Any gate can be implemented using either NOR or NAND gates.

Why is this important?


- When building a chip, easier to build one with all of the same gates.

<https://powcoder.com>

Add WeChat powcoder

  

Add WeChat powcoder

 

More than 2 Inputs?

AND/OR can take any number of inputs.


- AND = 1 if all inputs are 1.
- OR = 1 if any input is 1.
- Similar for NAND/NOR.

Assignment Project Exam Help

Can implement with multiple two-input gates or with single CMOS circuit.

<https://powcoder.com>

Add WeChat powcoder

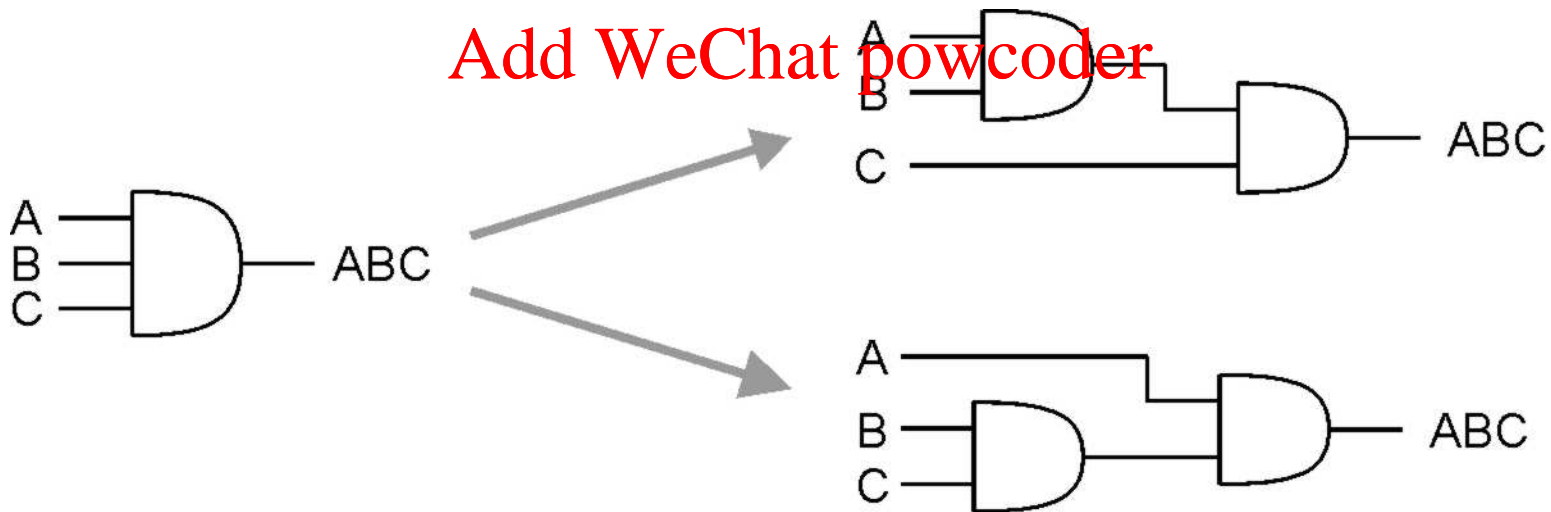

Circuit Design

Have a good idea. What kind of circuit might be useful?

Derive a truth table for this circuit

Derive a Boolean expression for the truth table

Build a circuit given the Boolean expression

- Building the circuit involves mapping the Boolean expression to actual gates. This part is easy.
- Deriving the Boolean expression is easy. Deriving a good one is tricky.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Given a circuit, isolate the rows in which the output of the circuit should be **true**

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\overline{A}BC = 1$$

$$A\overline{B}C = 1$$

$$AB\overline{C} = 1$$

$$ABC = 1$$

Given a circuit, isolate that rows in which the output of the circuit should be true

A product term that contains exactly one instance of every variable is called a minterm

Converting Truth Table to Boolean Expression

sensor
inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$$\bar{A}BC = 1$$

$$A\bar{B}C = 1$$

$$AB\bar{C} = 1$$

$$ABC = 1$$

$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Given the expressions for each row, build a larger Boolean expression for the entire table.

- This is a **sum-of-products (SOP)** form.

Canonical Forms

We have studied two canonical forms

1. Sum of Products (SoP)
2. Product of Sums (PoS)

How to convert to SoP from PoS (multiple through)

How to convert to PoS from SoP (complement, multiply through, complement via DeMorgan's)

Assignment Project Exam Help

<https://powcoder.com>

Note: $X' = \overline{X}$

Add WeChat powcoder

$$F = Y'Z' + XY'Z + XYZ'$$

$$F' = (Y+Z)(X'+Y+Z')(X'+Y'+Z)$$

$$= YZ + X'Y + X'Z \quad (\text{after lots of simplification})$$

$$F = (Y'+Z')(X+Y')(X+Z')$$

Formal Definition of Minterms

e.g., Minterms for 3 variables A,B,C

A	B	C	minterm
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$
0	0	1	m1 $\bar{A}\bar{B}C$
0	1	0	m2 $\bar{A}B\bar{C}$
0	1	1	m3 $\bar{A}BC$
1	0	0	m4 $A\bar{B}\bar{C}$
1	0	1	m5 $A\bar{B}C$
1	1	0	m6 $AB\bar{C}$
1	1	1	m7 ABC

- A product term in which all variables appear once, either complemented or uncomplemented (i.e., an entry in the truth table).

- Each minterm evaluates to 1 for exactly one variable assignment, 0 for all others.


- Denoted by mX where X corresponds to the variable assignment for which $mX = 1$.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

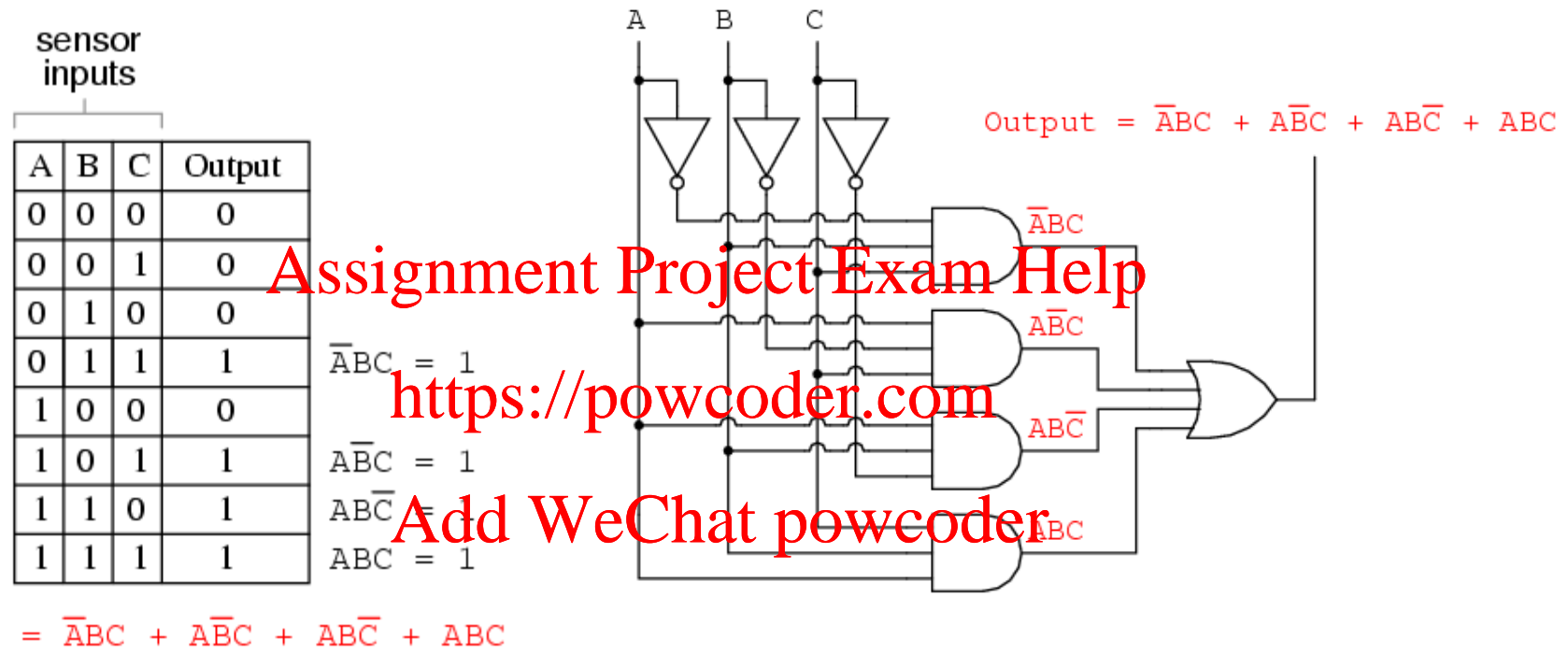Converting Truth Table to Boolean Expression



Finally build the circuit.

- Problem: SOP forms are often not minimal.
- Solution: Make it minimal. We'll go over two ways.

First Approach: Algebraic

Simply use the rules of Boolean logic


$$\begin{aligned}
 &\overline{A}BC + \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC \\
 &\quad \downarrow \text{Factoring } \mathbf{BC} \text{ out of 1}^{\text{st}} \text{ and 4}^{\text{th}} \text{ terms} \\
 &BC(\overline{A} + A) + \overline{A}\overline{B}C + A\overline{B}\overline{C} \\
 &\quad \downarrow \text{Applying identity } \mathbf{A + \overline{A} = 1} \\
 &BC(1) + \overline{A}\overline{B}C + A\overline{B}\overline{C} \\
 &\quad \downarrow \text{Applying identity } \mathbf{1A = A} \\
 &BC + \overline{A}\overline{B}C + A\overline{B}\overline{C} \\
 &\quad \downarrow \text{Factoring } \mathbf{B} \text{ out of 1}^{\text{st}} \text{ and 3}^{\text{rd}} \text{ terms} \\
 &B(C + \overline{A}\overline{C}) + \overline{A}\overline{B}C \\
 &\quad \downarrow \text{Applying rule } \mathbf{A + \overline{A}B = A + B} \text{ to the } \mathbf{C + \overline{A}\overline{C}} \text{ term} \\
 &B(C + A) + \overline{A}\overline{B}C \\
 &\quad \downarrow \text{Distributing terms} \\
 &BC + AB + \overline{A}\overline{B}C \\
 &\quad \downarrow \text{Factoring } \mathbf{A} \text{ out of 2}^{\text{nd}} \text{ and 3}^{\text{rd}} \text{ terms} \\
 &BC + A(B + \overline{B}C) \\
 &\quad \downarrow \text{Applying rule } \mathbf{A + \overline{A}B = A + B} \text{ to the } \mathbf{B + \overline{B}C} \text{ term} \\
 &BC + A(B + C) \\
 &\quad \downarrow \text{Distributing terms} \\
 &BC + AB + AC \\
 &\quad \text{or} \\
 &AB + BC + AC
 \end{aligned}$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


The Result

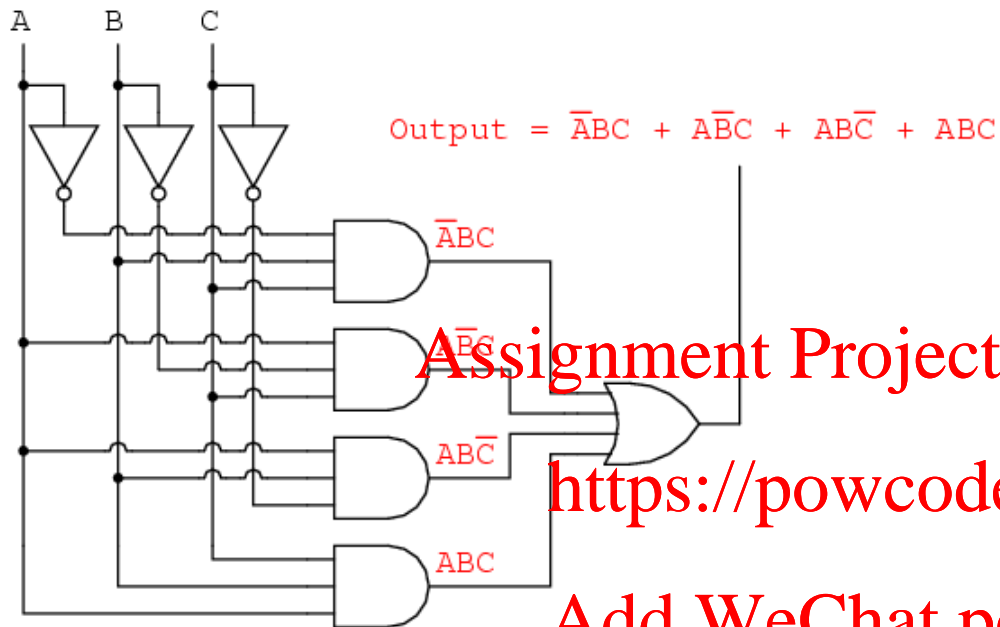

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

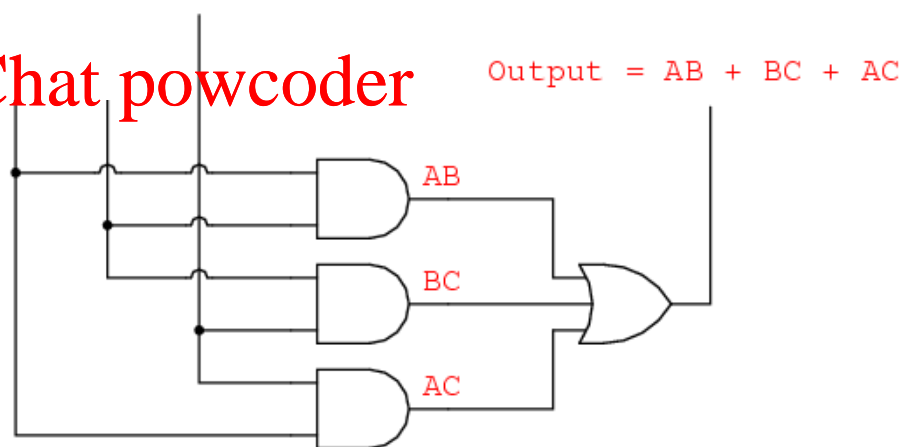

Decoder


n inputs, 2^n outputs

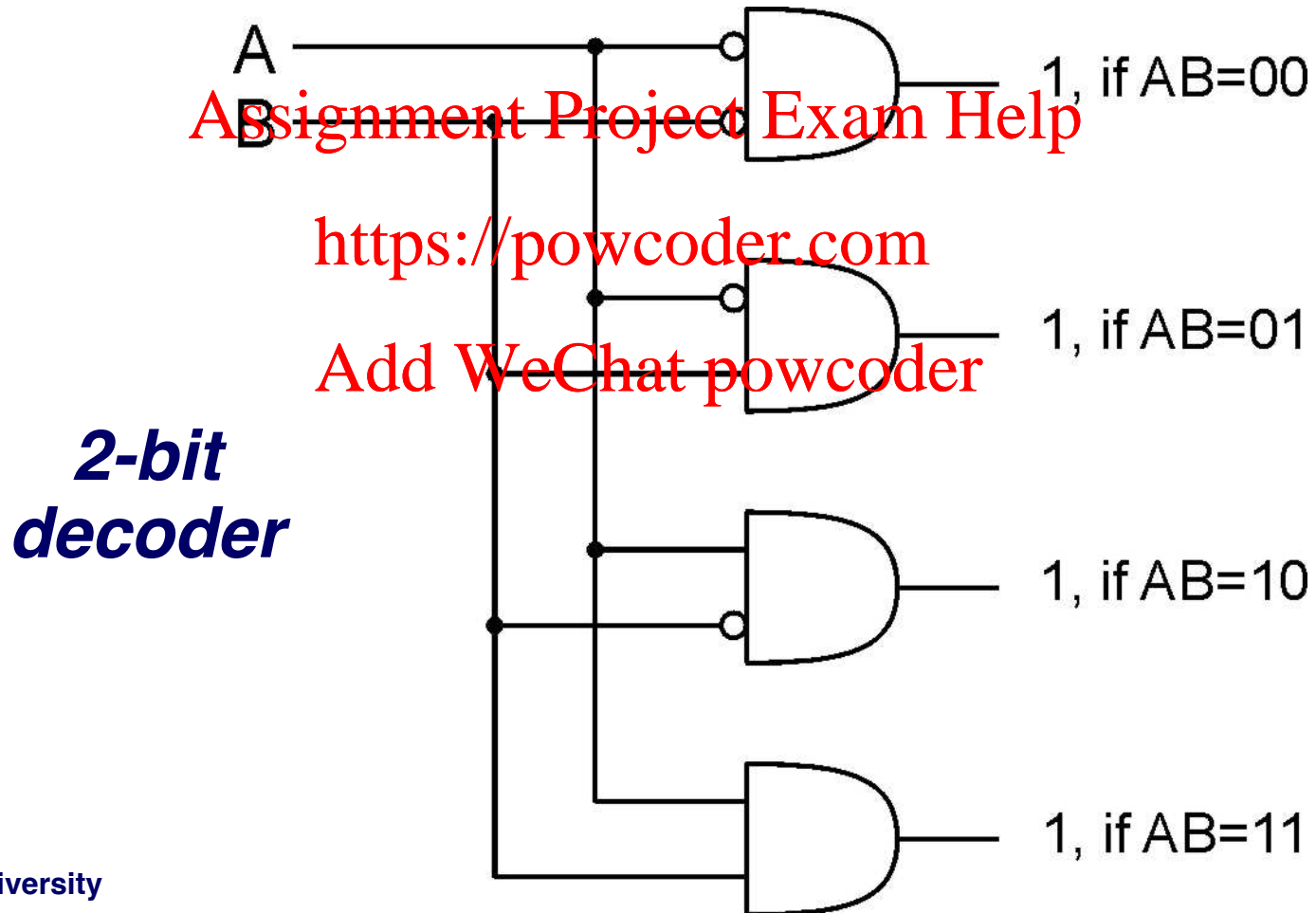- exactly one output is 1 for each possible input pattern



Decoder Circuits

 
Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$



"Standard" Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Decoder Example

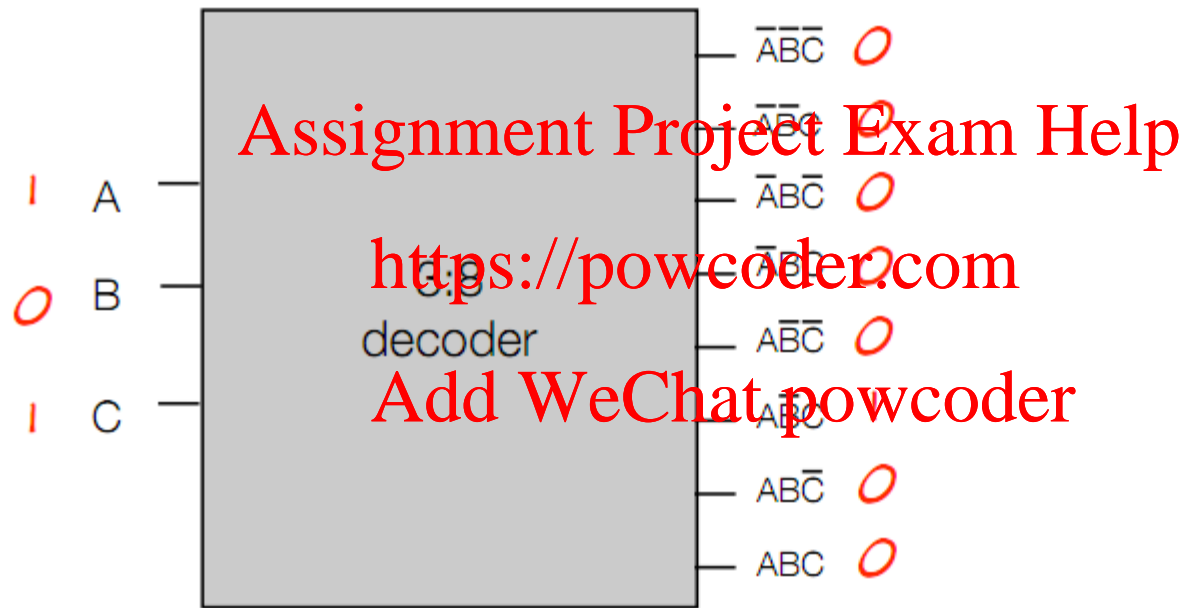
Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$




e.g., $ABC = 101$ ($i=5$)

"Standard" Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Internal 2:4 Decoder Design

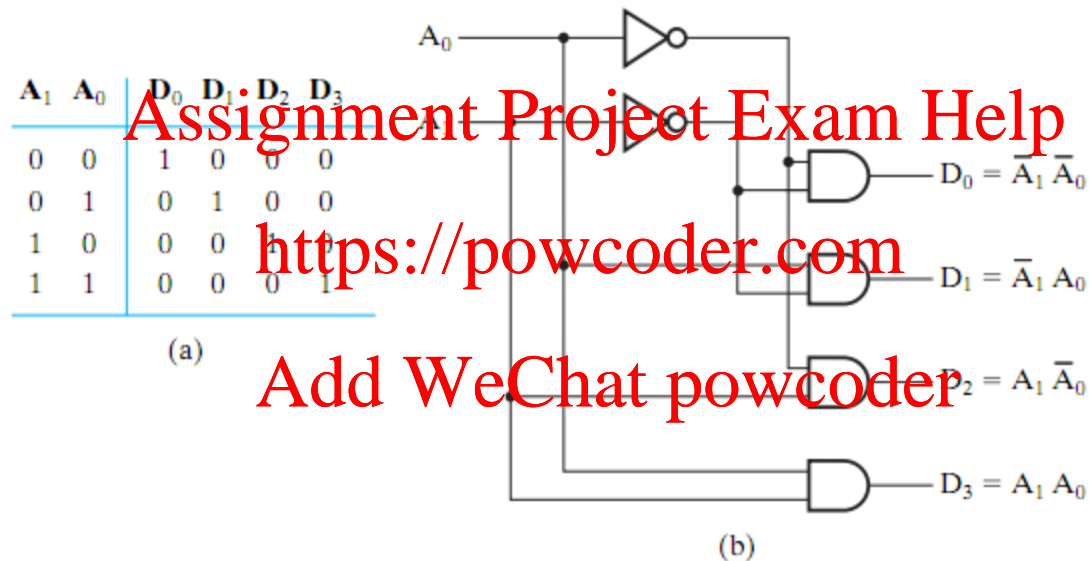


2:4 Decoder from 1:2 Decoders

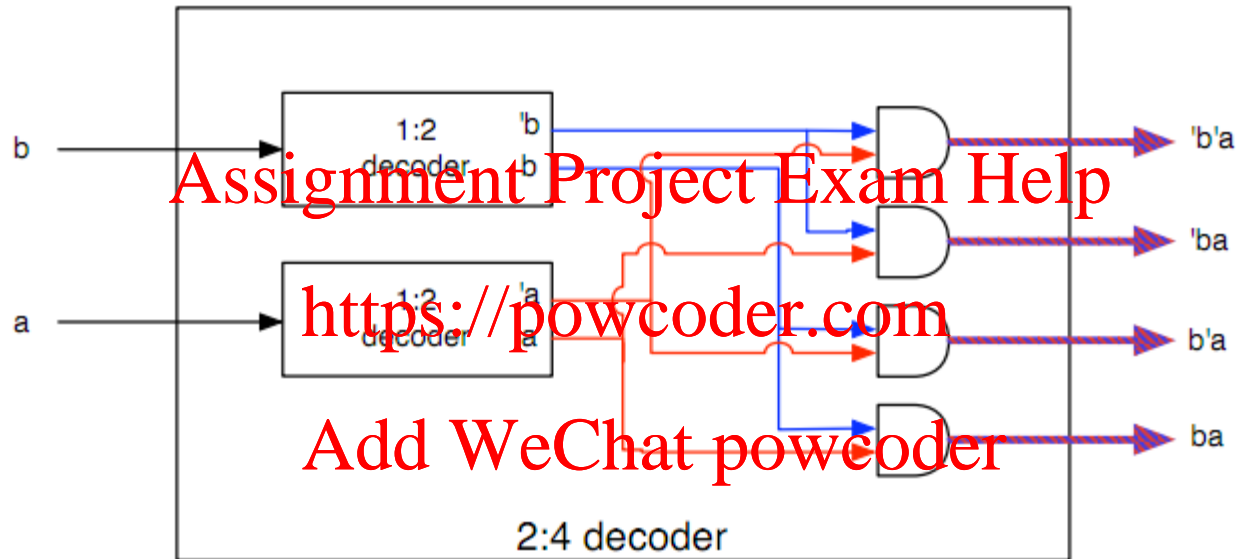

*Can build 2:4 decoder out of two 1:2 decoders
(and some additional circuitry)*

Hierarchical 3:8 Decoder

 

Encoder: Inverse of Decoder

Inverse of decoder: converts m bit input to n bit output
($n \leq m$)

□ **TABLE 3-7**
Truth Table for Octal-to-Binary Encoder


Inputs								Outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

© 2008 Pearson Education, Inc.
M. Morris Mano & Charles R. Kime
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

Multiplexer (MUX)

n -bit selector and 2^n inputs, one output

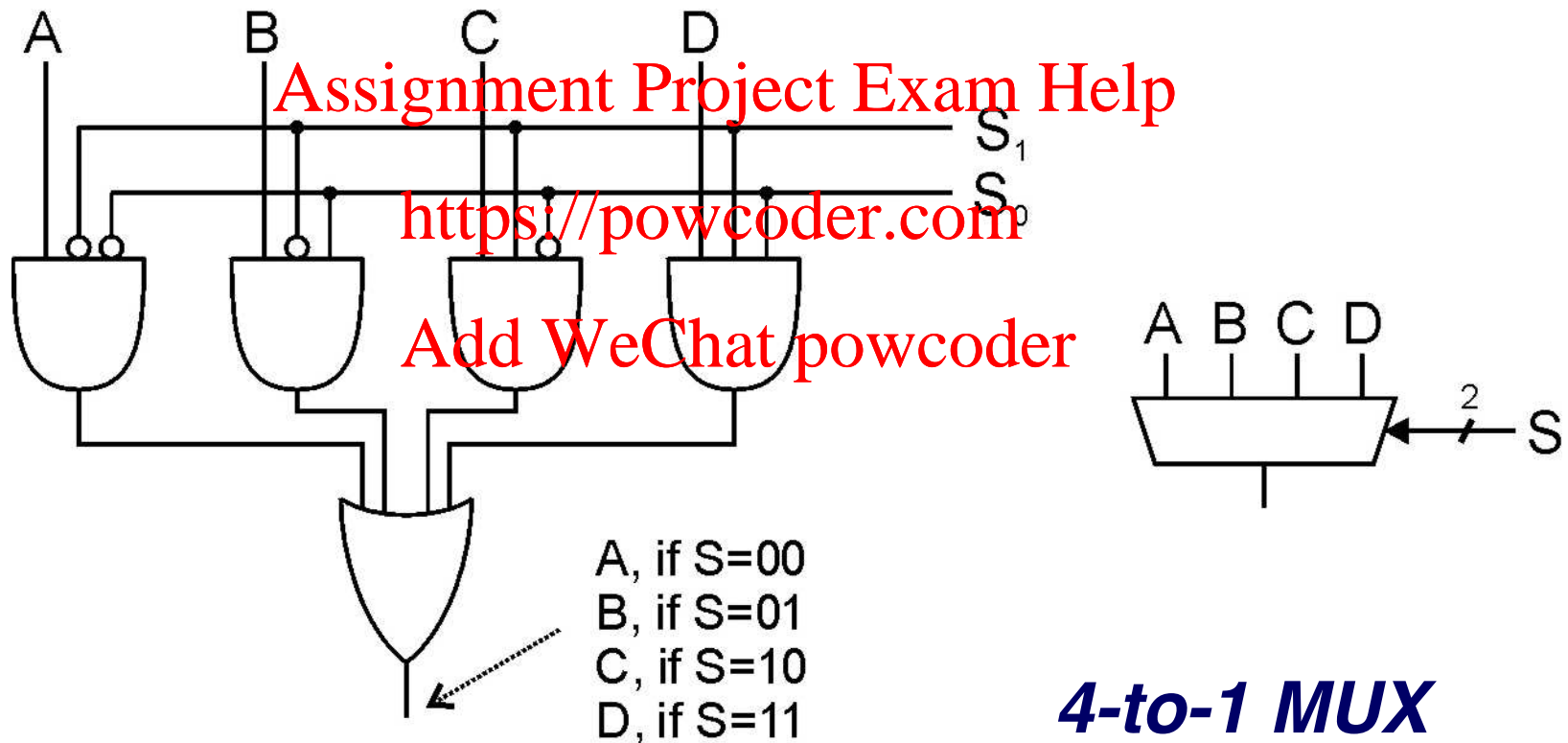- output equals one of the inputs, depending on selector



Multiplexers (Muxes)

Combinational circuit that selects binary information from many inputs to one output

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




n selection bits
indicate (in binary) which input feeds to the output

Functions with Decoders or Muxes

- e.g., $F = A\bar{C} + BC$

A	B	C	minterm	F
0	0	0	$\bar{A}\bar{B}\bar{C}$	0
0	0	1	$\bar{A}\bar{B}C$	0
0	1	0	$\bar{A}B\bar{C}$	0
0	1	1	$\bar{A}BC$	1
1	0	0	$A\bar{B}\bar{C}$	1
1	0	1	$A\bar{B}C$	0
1	1	0	$AB\bar{C}$	1
1	1	1	ABC	1

 

- Decoder: OR minterms for which F should evaluate to 1
- MUX: Feed in the value of F for each minterm

Can we do it a Smaller Mux?

Can actually use a smaller mux with a trick:

$$F = A\bar{C} + BC$$


Look at the rows below, A & B have the same value, C iterates between 0 & 1

For the pair of rows, F either equals 0 or 1, C or not(C)

A	B	C	minterm	F
0	0	0	$\bar{A}\bar{B}\bar{C}$	0
0	0	1	$\bar{A}\bar{B}C$	0
0	1	0	$\bar{A}B\bar{C}$	0
0	1	1	$\bar{A}BC$	1
1	0	0	$A\bar{B}\bar{C}$	1
1	0	1	$A\bar{B}C$	0
1	1	0	$AB\bar{C}$	1
1	1	1	ABC	1

<https://powcoder.com>


Add WeChat powcoder

 

Another Example

- e.g., $F = \bar{A}C + \bar{B}\bar{C} + A\bar{C}$

Assignment Project Exam Help

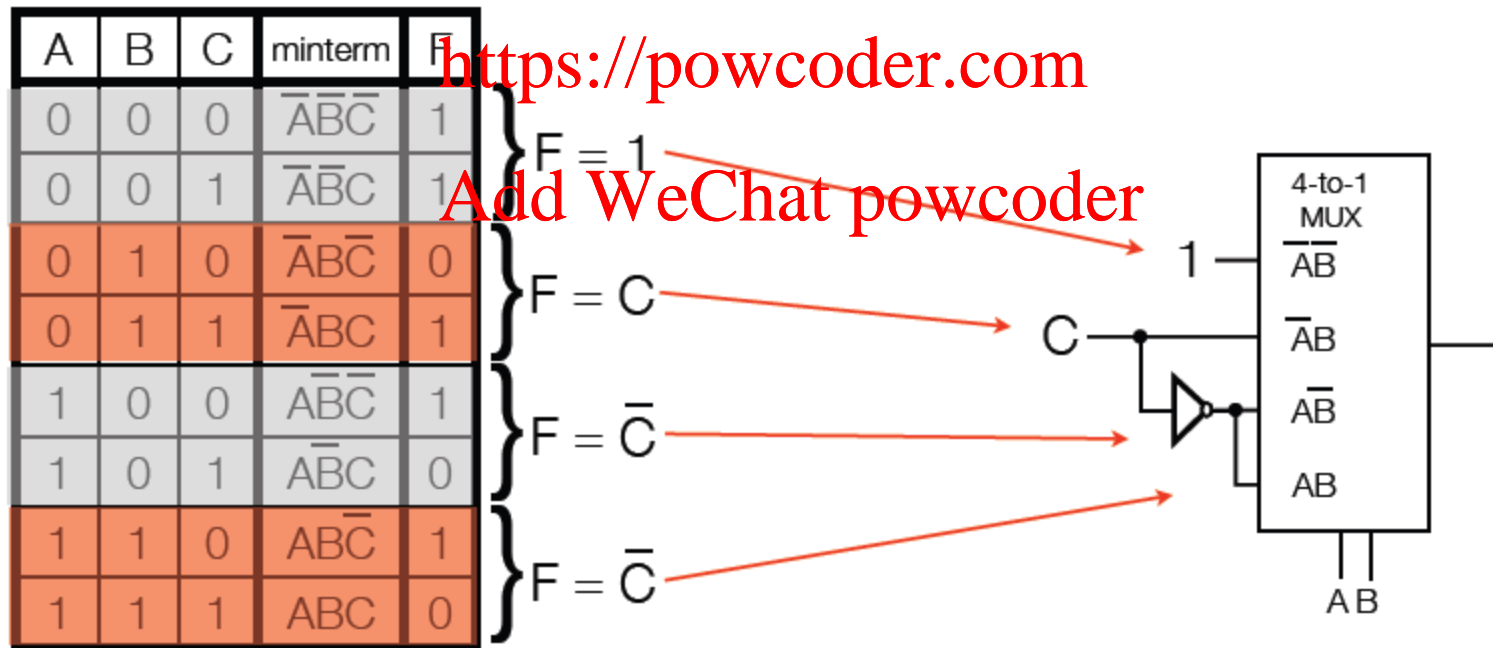

Where are we?

We have already seen

- Basic gates: AND, NOT, OR
- Building blocks: Decoder and Multiplexer
- Implement circuits from truth tables
- We know: (a) minterm (b) Sum of products
- We know basic identities

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Implement A+B

With Multiplexers

(1) Using 2:1 mux

Assignment Project Exam Help

<https://powcoder.com>

(2) Using 4:1 mux

Add WeChat powcoder

With Decoders

(1) Using a 2:4 decoder

Half Adder

Add two bits and produce a sum and a carry.

How do we go about building the circuit?


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Full Adder

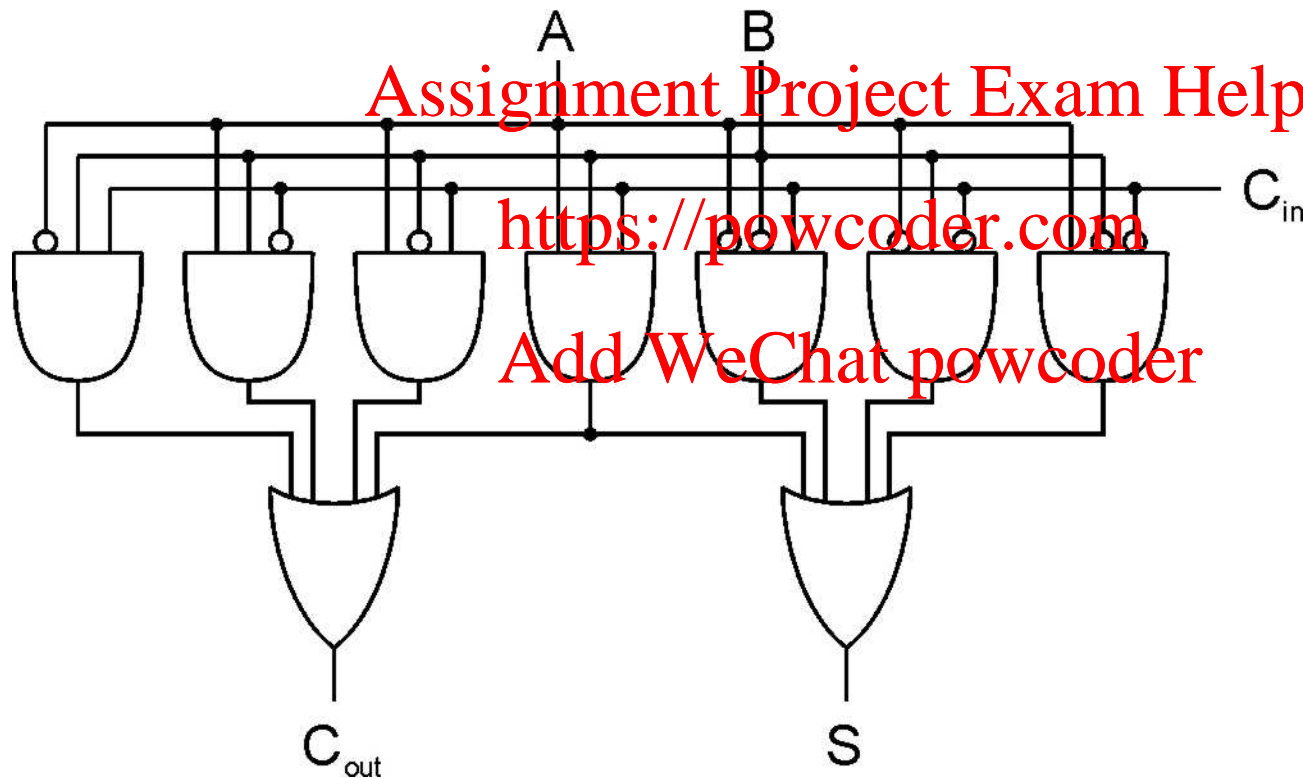Add two bits and carry-in,
produce one-bit sum and carry-out.



A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

ignment Project Exam Help
Full Adder Full Adder
Add WeChat powcoder



Karnaugh Maps or K-Maps

K-maps are a graphical technique to view minterms and how they relate.

The “map” is a diagram made up of squares, with each square representing a minterm.


Minterms resulting in a “1” are marked as “1”, all others are marked “0”

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


2 Variable K-Map

 

<https://powcoder.com>

Add WeChat powcoder

2 Variable K-Map

 


<https://powcoder.com>

Add WeChat powcoder

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

A \ B	0	1
0		
1		

2 Variable K-Map

 


<https://powcoder.com>

Add WeChat powcoder

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1


A \ B	0	1
0	0	1
1	0	1

Finding Commonality

 


Out = B

Add WeChat powcoder

 


Finding the “best” solution

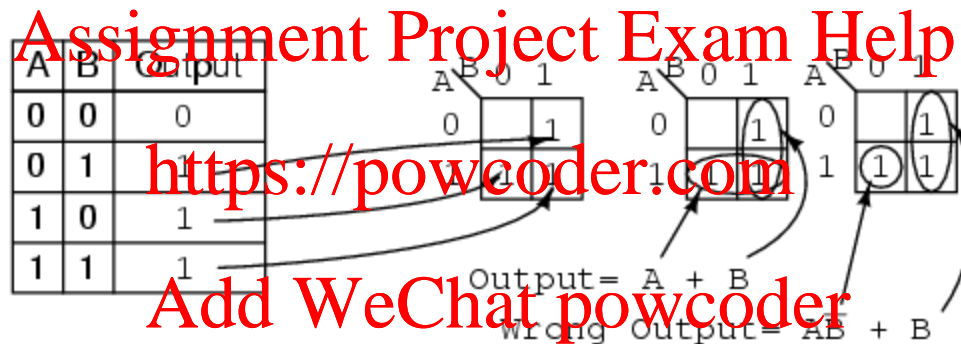

Grouping become simplified products.

Both are “correct”. “A+B” is preferred.

Simplify Example

 


Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


Simplify Example

 

<https://powcoder.com>

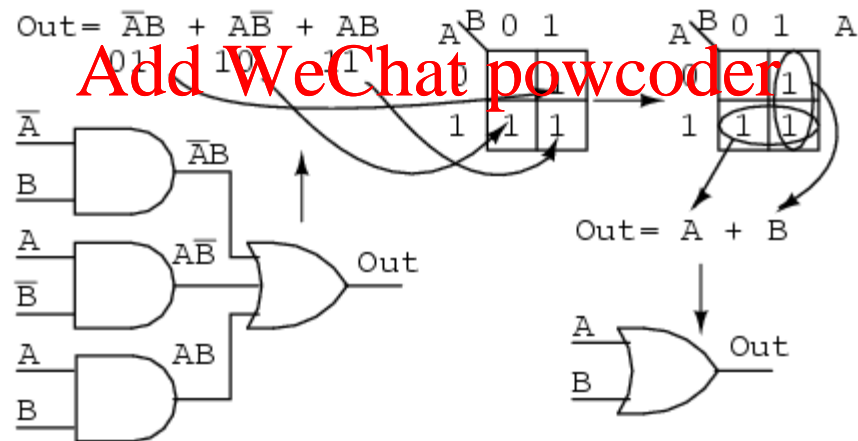

3 Variable K-Maps

 

<https://powcoder.com>

- Note in higher maps, several variables occupy a given axis
- The sequence of 1s and 0s follow a Gray Code Sequence.
- Grey code is a number system where two successive values differ only by 1-bit

3 Variable K-Maps

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}				
A				

	00	01	11	10
0				
1				

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C}$$

	00	01	11	10
0	1	1		
1				

$$\text{Out} = \overline{A}\overline{B}$$

3 Variable K-Maps

 


Assignment Project Exam Help

<https://powcoder.com>


$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC$$

Add WeChat powcoder

 

$$\text{Out} = \overline{A}$$

3 Variable K-Maps

 


Assignment Project Exam Help

<https://powcoder.com>


$$\text{Out} = ABC + A\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C$$

Add WeChat powcoder

 

$$\text{Out} = C$$

3 Variable K-Maps

 


Assignment Project Exam Help

<https://powcoder.com>



$$\text{Out} = \bar{A} + B$$

3 Variable K-Maps

 


Assignment Project Exam Help


<https://powcoder.com>

$$\text{Out} = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C}$$

Add WeChat powcoder

 

Back to our earlier example.....

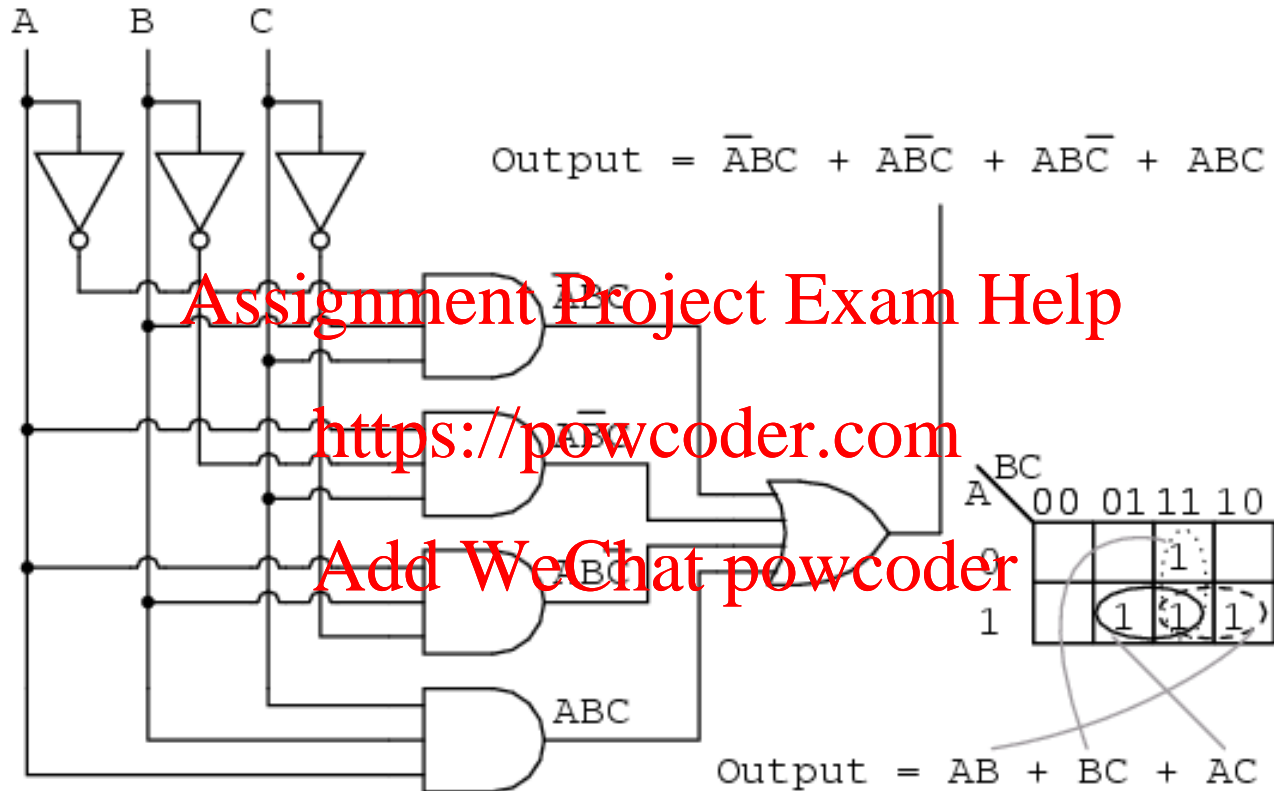

The K-map and the algebraic produce the same result.

Up... up... and let's keep going

Assignment Project Exam Help

Diagram showing a 4x4 Karnaugh map for variables A, B, C, and D. The map is empty. Brackets indicate the variable ranges: A for rows (00, 01, 11, 10), B for columns (00, 01, 11, 10), C for the first two columns (00, 01), and D for the last two columns (11, 10).

<https://powcoder.com>

$$\text{Out} = ABCD + ABC\bar{D} + AB\bar{C}D + AB\bar{C}\bar{D}$$

Add WeChat powcoder

Diagram showing a 4x4 Karnaugh map for variables A, B, C, and D. The map has 1s in the four corners: (A=0, B=0, C=0, D=0), (A=0, B=0, C=1, D=1), (A=1, B=1, C=0, D=0), and (A=1, B=1, C=1, D=1). Red dashed lines connect these 1s in a square pattern. To the right is a 3D cube diagram with the same four corners highlighted by a red dashed box. Below the maps is the simplified expression $\text{Out} = \bar{B}\bar{D}$.

Few more examples

Diagram of a 4x4 Karnaugh map for variables A, B, C, and D. The map is labeled with A and B on the vertical axis and C and D on the horizontal axis. The vertical axis is labeled A/B with values 00, 01, 11, 10. The horizontal axis is labeled C/D with values 00, 01, 11, 10. Brackets indicate the grouping of variables: A (rows), B (columns), C (columns), and D (columns).

Assignment Project Exam Help

<https://powcoder.com>

$$\text{Out} = \overline{A}BCD + \overline{A}BC\overline{D} + A\overline{B}CD + ABCD$$

Add WeChat powcoder

Diagram of a 4x4 Karnaugh map for variables A, B, C, and D. The map is labeled with A and B on the vertical axis and C and D on the horizontal axis. The vertical axis is labeled A/B with values 00, 01, 11, 10. The horizontal axis is labeled C/D with values 00, 01, 11, 10. The map shows the following values:

00	1		1
01			
11		1	
10	1		

$$\text{Out} = \overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{D} + ABCD$$

Few more examples

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$$\begin{aligned} \text{Out} = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD \\ & + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD \\ & + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + AB\bar{C}\bar{D} + ABC\bar{D} \\ & + AB\bar{C}D + ABCD \end{aligned}$$

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

$$\text{Out} = \bar{A}\bar{C} + \bar{A}D + B\bar{C} + BD$$

Don't Care Conditions

- Let $F = AB + \bar{A}\bar{B}$
- Suppose we know that a disallowed input combo is $A=1, B=0$
- Can we replace F with a simpler function G whose output matches for all inputs we do care about?
- Let H be the function with Don't-care conditions for obsolete inputs

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

Inputs will
not occur →

<https://powcoder.com>

Add WeChat powcoder

$$G = AB + \bar{B}$$

- Both F & G are appropriate functions for H
- G can substitute for F for valid input combinations

Don't Cares can Greatly Simplify Circuits


Sometimes “don't cares” greatly simplify circuitry

Assignment Project Exam Help
<https://powcoder.com>
 Add WeChat powcoder

		D			
		1	X	X	X
		X	1	X	X
		0	0	1	X
A		0	0	X	1
		C			

$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + ABCD + A\bar{B}C\bar{D} \text{ vs. } \bar{A} + C$$

Design Example

 

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


e.g., what outputs
“lights up” when input
 $V=4$?

Input					Output						
Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	0	1	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Design Example

 

 For what values does
output 'f' light up for?





Input Output

Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Design Example

 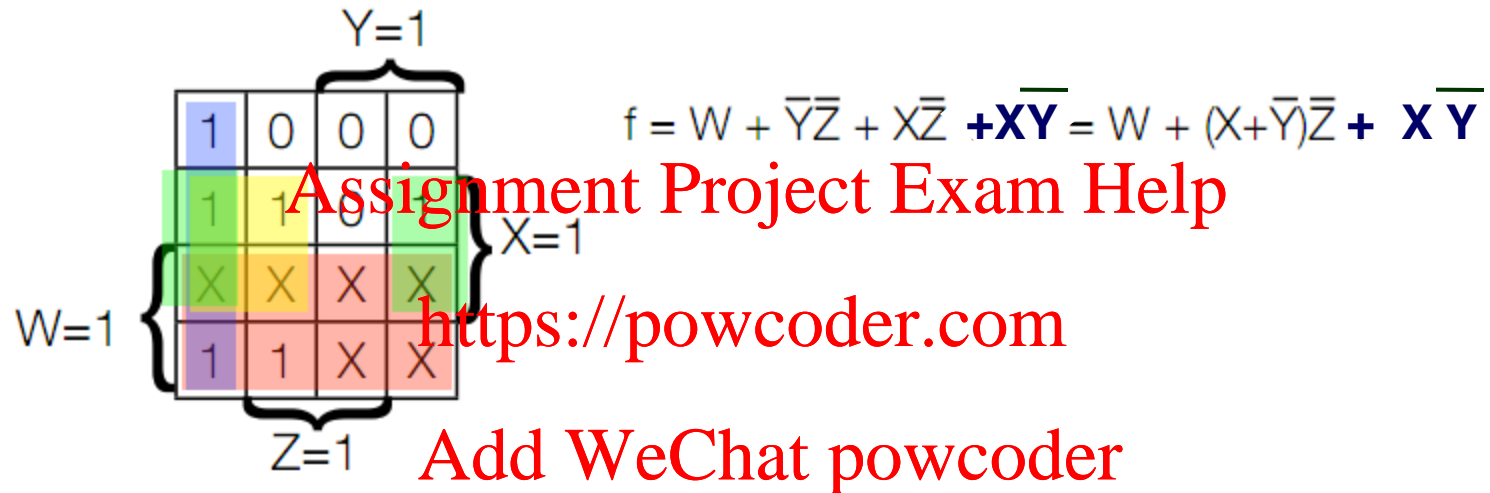We will do f, but you should be able to design a-e as well



Combinational Circuits


Stateless circuits

Outputs are function of inputs only

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Time and State

SEQUENTIAL CIRCUITS

How are Sequential Circuits different from Combinational Circuits?

Outputs of sequential logic depend on both current and prior values – it has memory

Definitions: **Assignment Project Exam Help**

State: all the information about a circuit to explain its future behavior
<https://powcoder.com>

Add WeChat powcoder

Latches and flip-flops: state elements that store one bit of state

Synchronous sequential elements: combinational logic followed by a bank of flip-flops

Enabler Circuits

Output is “enabled” ($F=A$) only when input ‘ENABLE’ signal is asserted ($EN=1$)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



EN	F
0	0
1	A



(b)

EN	F
0	1
1	A

Bistable Circuits

Fundamental building blocks of other elements


No inputs

Two outputs (Q and Q')

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Bistable Circuit Analysis

Consider all the cases

- Consider the two possible cases:


- $Q = 0$: then $\bar{Q} = 1$ and $Q = 0$ (consistent)

Assignment Project Exam Help

<https://powcoder.com>

- $Q = 1$: then $\bar{Q} = 0$ and $Q = 1$ (consistent)


Add WeChat powcoder

 

Bistable circuit stores 1 bit of state (Q, or Q')


But there are no inputs to control state

Set/Reset Latch

 

S/R Latch Analysis


- $S = 1, R = 0$: then $Q = 1$

 

Assignment Project Exam Help

<https://powcoder.com>

- $S = 0, R = 1$: then $Q = 0$

 

set


Add WeChat powcoder

reset


Copyright © 2007 Elsevier

S/R Latch Analysis

- $S = 0, R = 0$: then $Q = Q_{prev}$

 

 - $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$



Copyright © 2007 Elsevier

S/R Latch Symbol

Set operation – makes output 1 ($S = 1, R = 0, Q = 1$)

Reset operation – makes output 0 ($S = 0, R = 1, Q = 0$)


What about invalid state? ($S = 1, R = 1$)

Assignment Project Exam Help

<https://powcoder.com>

SR Latch

Add WeChat powcoder

 

D Latch

Two inputs (C and D)

C: controls when the output changes

D (data input): controls what the output changes to


When $C = 1$, D passes through to Q (transparent latch)

When $C = 0$, Q holds previous value (opaque latch)


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

D Latch Internal Circuit

 

Assignment Project Exam Help

<https://powcoder.com>

C	D	\bar{D}	S	R	Q	\bar{Q}
0	X					
1	0					
1	1					

Add WeChat powcoder

How to Coordinate with Multiple Components?

But how do we coordinate computations and the changing of state values across lots of different parts of a circuit?

Assignment Project Exam Help

We use CLOCKING (eg. 2.6GHz clock on Intel processors)

On each clock pulse, combinational computations are performed, and results stored in latches


<https://powcoder.com>

Add WeChat powcoder

How to introduce clocks into latches?


Flip-flops: Latches on a Clock

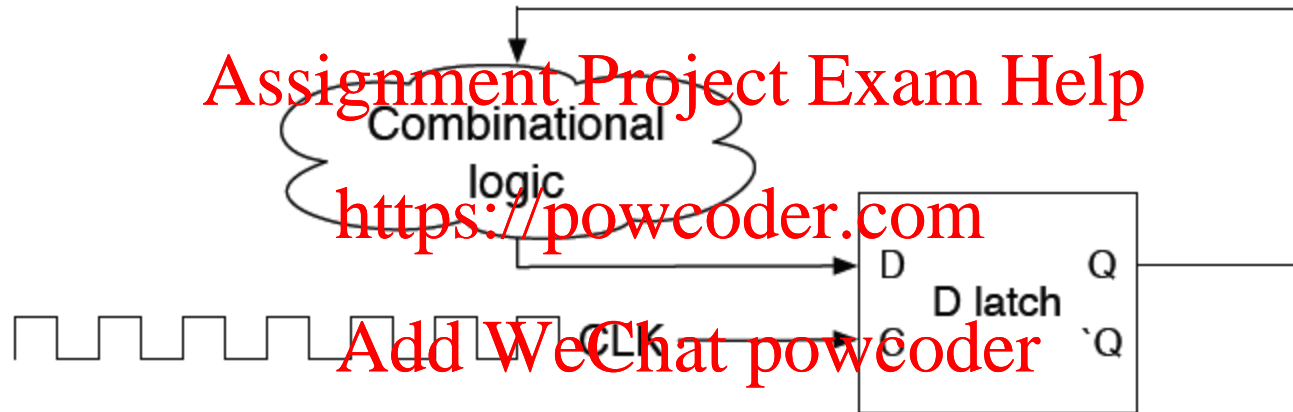A straightforward latch is not safely synchronous (or predictably synchronous)



Flip-flops designed so that outputs will NOT change within a single clock pulse

D Flip-Flop

 

When CLK is 0

- master is enabled (N1 obtains the value input to the master)
- slave is disabled (Old output is still output)

When CLK is 1

- then master is disabled (N1 is the old value)
- Slave is enabled, it copies N1 into output


D Flip-Flop Summary

Two inputs: Clk, D

Function

- The flip-flop samples D on rising clock edge
- When clock goes from 0 to 1, D passes through Q
- Otherwise, Q holds its value
- Q only changes on rising clock edge
- Flip-flop is called “edge-triggered” because it is activated only on the clock edge

D Flip-Flop
Symbols

 


Flip-Flop versus Latch



Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

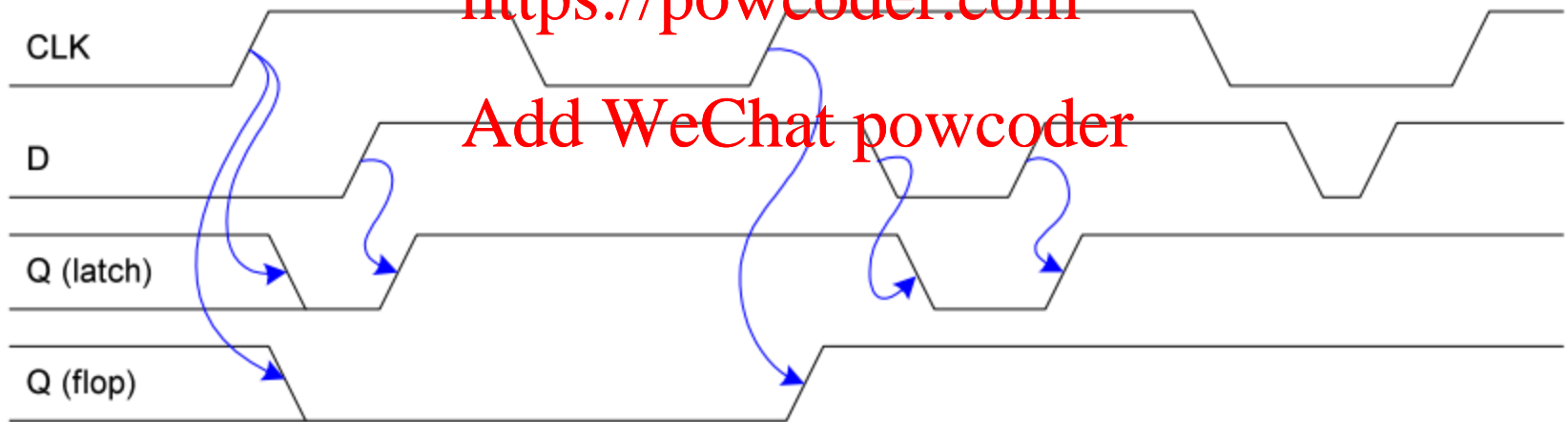

Latch outputs change at any time, flip-flops only during clock transitions

Registers

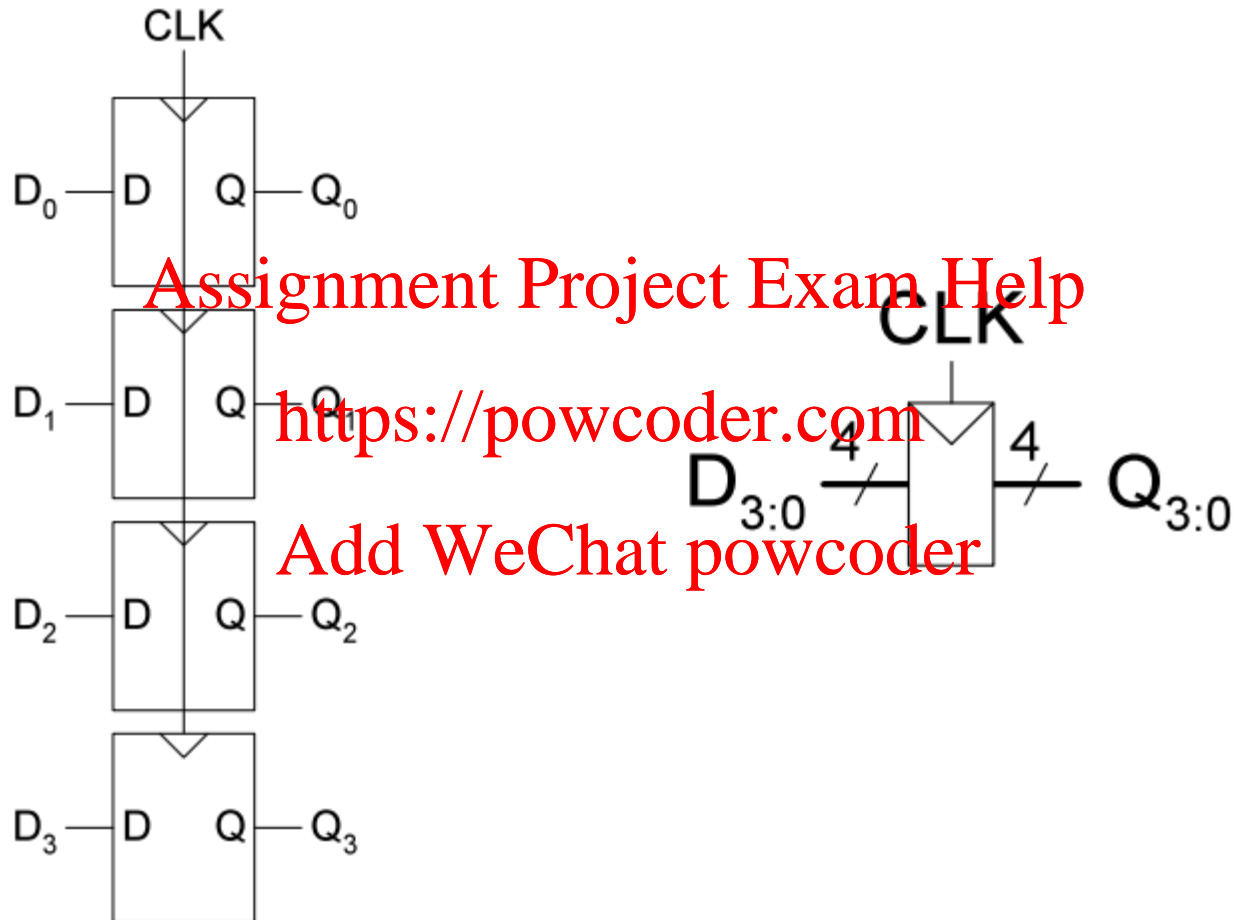

Finite State Machines

FSM = State register + combinational logic



Stores the next state and loads the next state at clock edge

Computes the next state and computes the outputs

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

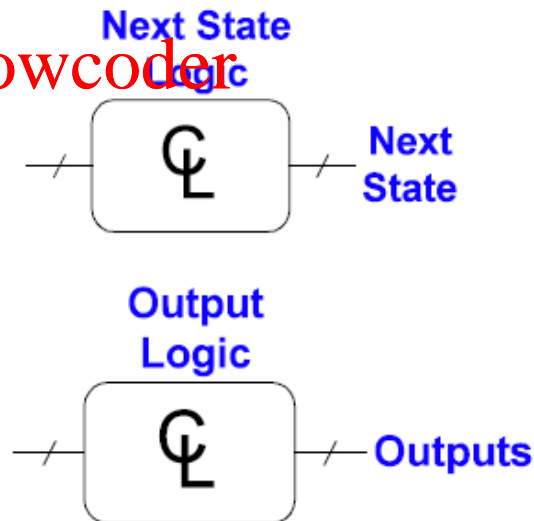 


Traffic Light Controller Example

- Traffic sensors: T_A , T_B (TRUE when there is traffic)

Assignment Project Exam Help


- Lights: L_A , L_B

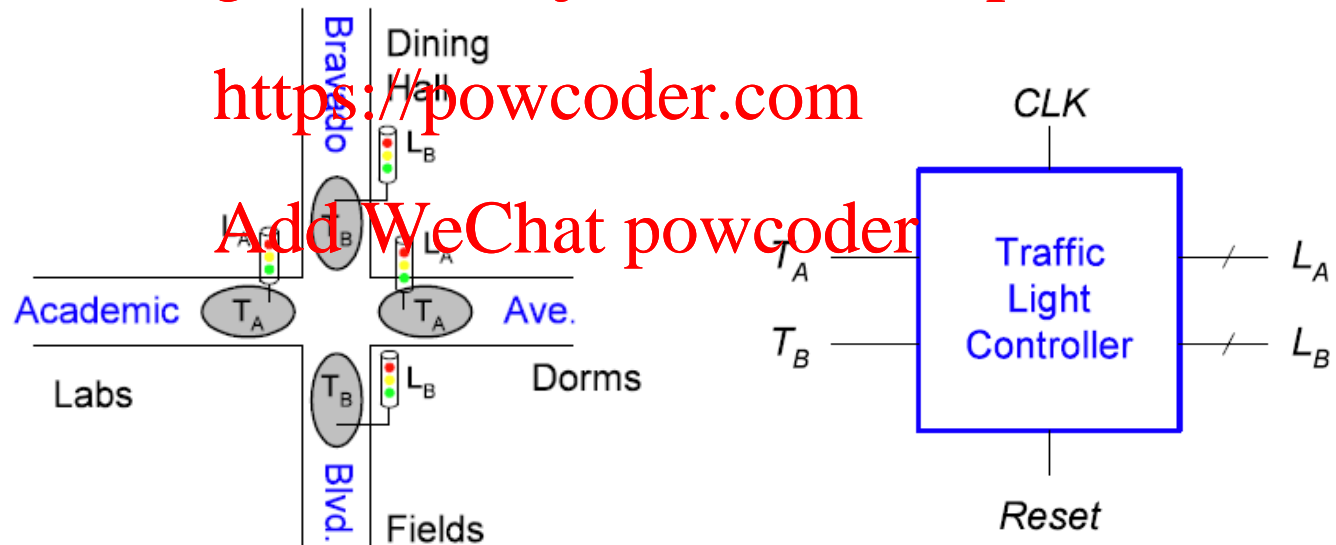

FSM State Transition Diagram

- States: Circles

- Transitions: Arcs

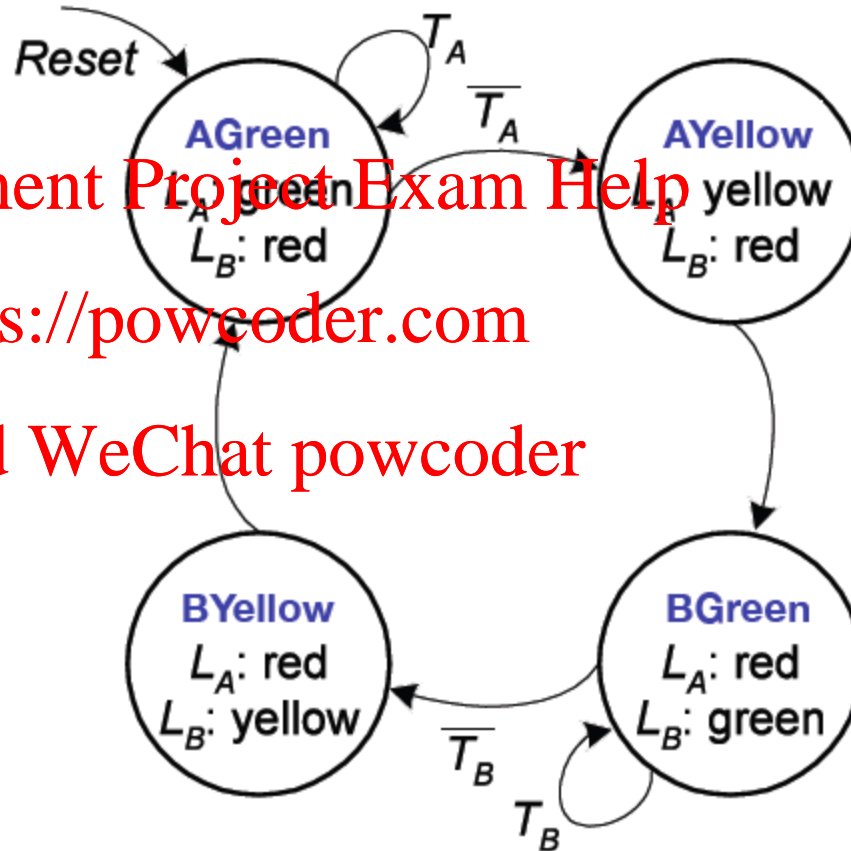

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

FSM State Transition Table

State transitions from diagram can be rewritten in a state transition table

(S = current state, S' = next state)

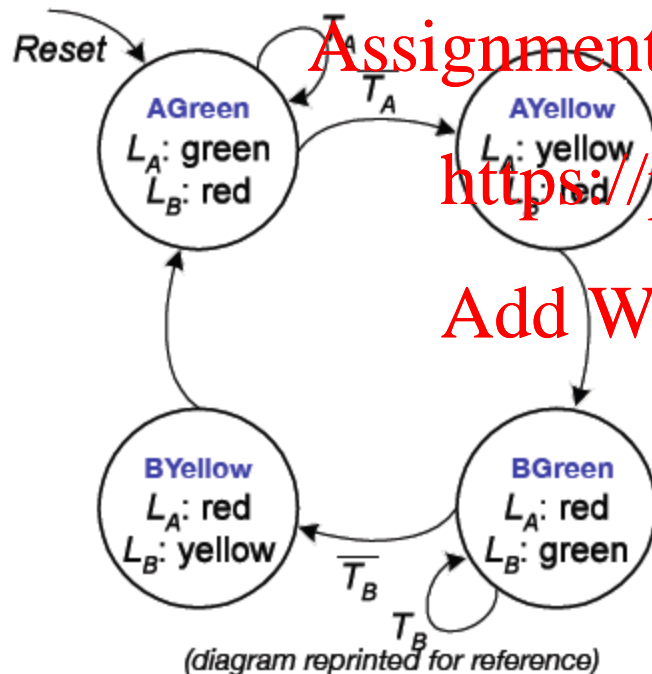

Current State S	Inputs		Next State S'
	T_A	T_B	
AGreen	0	X	AYellow
AGreen	1	X	AGreen
AYellow	X	X	BGreen
BGreen	X	0	BYellow
BGreen	X	1	BGreen
BYellow	X	X	AGreen

Encoded State Transition Table

After selecting a state encoding, the symbolic states in the transition table can be realized with current state/next state bits

State	Encoding	
	S1	S0
AGreen	0	0
AYellow	0	1
BGreen	1	0
BYellow	1	1

Assignment Project Exam Help

<https://powcoder.com>

Current State S	Encoded Current State		Inputs		Next State S'	Encoded Next State	
	S1	S0	TA	TB		S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

Computing Next State Logic

Current State	Encoded Current State		Inputs		Next State	Encoded Next State	
S	S1	S0	TA	TB	S'	S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

From K-maps, figure out expressions for the next state:

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$

FSM Output Table

FSM output logic is computed in similar manner as next state logic

In this system, output is a function of current state (Moore machine)

Alternative – Mealy machine (output function of both current state and inputs, though we won't cover this in class)

Assignment Project Exam Help

output encoding

Output	Encoding	
Green	0	0
Yellow	0	1
Red	1	0

output truth table


State	LA		LB			
	S1	S0	LA1	LA0	LB1	LB0
AGreen	0	0	0	0	1	0
AYellow	0	1	0	1	1	0
BGreen	1	0	1	0	0	0
BYellow	1	1	1	0	0	1

- Compute output bits as function of state bits

$$L_{A1} = S_1; L_{A0} = \overline{S_1} S_0$$

$$L_{B1} = \overline{S_1}; L_{B0} = S_1 S_0$$

State Register: Assume D-FF

 

FSM: Figure out Next State Logic


$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

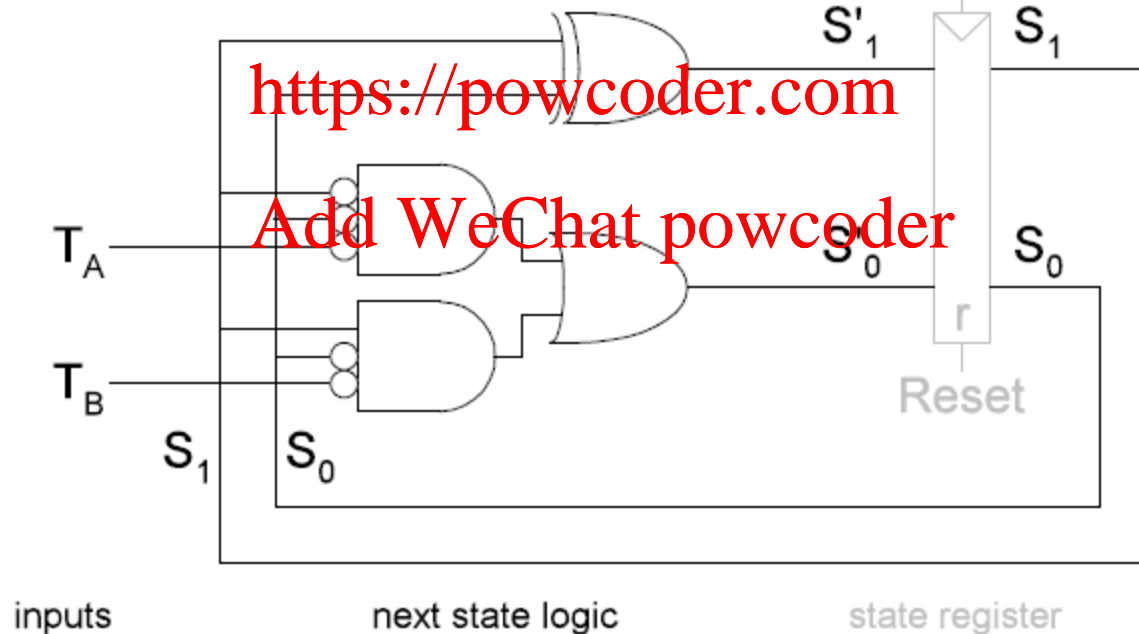

FSM: Figure out Output Logic


$$L_{A1} = S_1; L_{A0} = \overline{S_1} S_0$$

$$L_{B1} = \overline{S_1}; L_{B0} = S_1 S_0$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

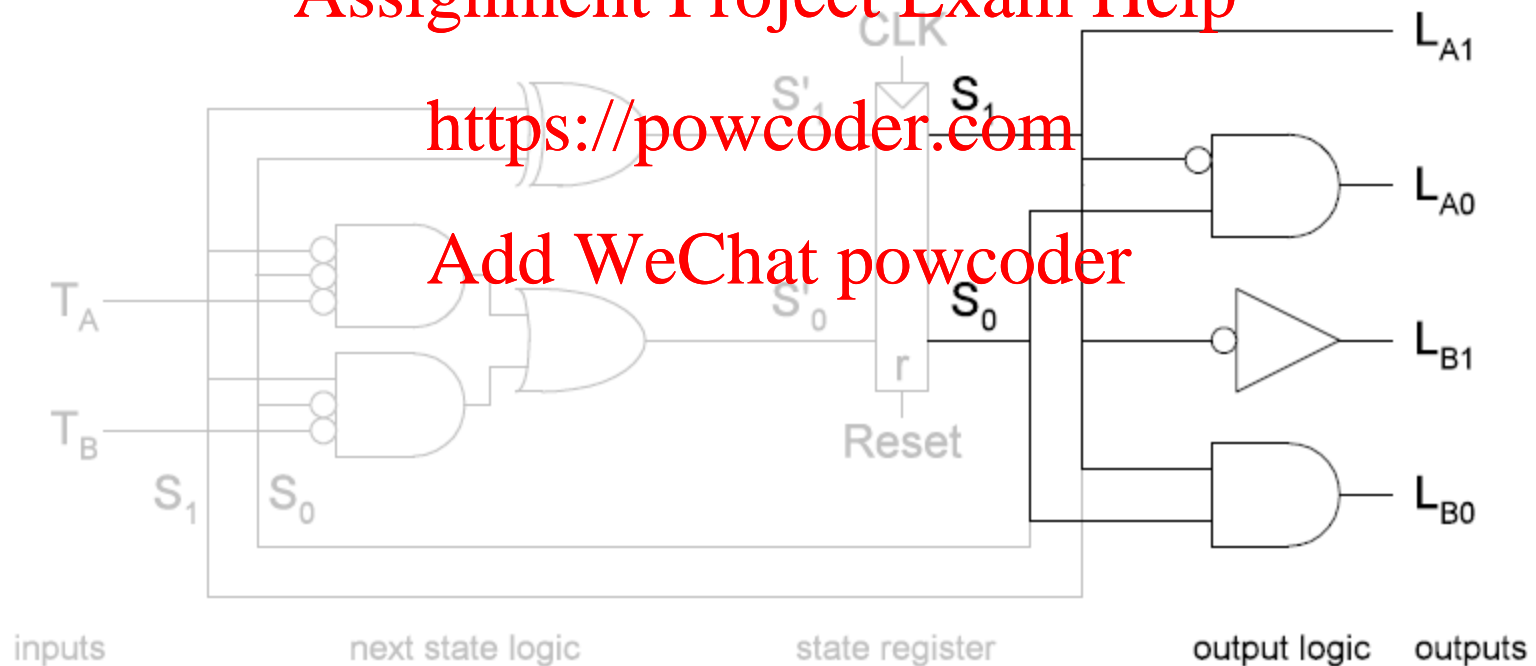

FSM Example 2

Design an FSM that detects a stream of three or more consecutive 1s on an input stream

Input:


0 1 1 0 1 0 1 1 0 1 1 1 0 1 ...

Output:

0 0 0 1 0 0 0 0 0 0 0 0 1 0 0 ...

Add WeChat powcoder

 Finite State Machine for the 3 1's problem



FSM Truth Table

Truth Table for Next State (AN and BN are next states)

A	B	X	AN	BN
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Encoding

	A	B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

We need two bits
to encode 4 states
(lets call these bits A & B)

FSM with D-Flip Flops

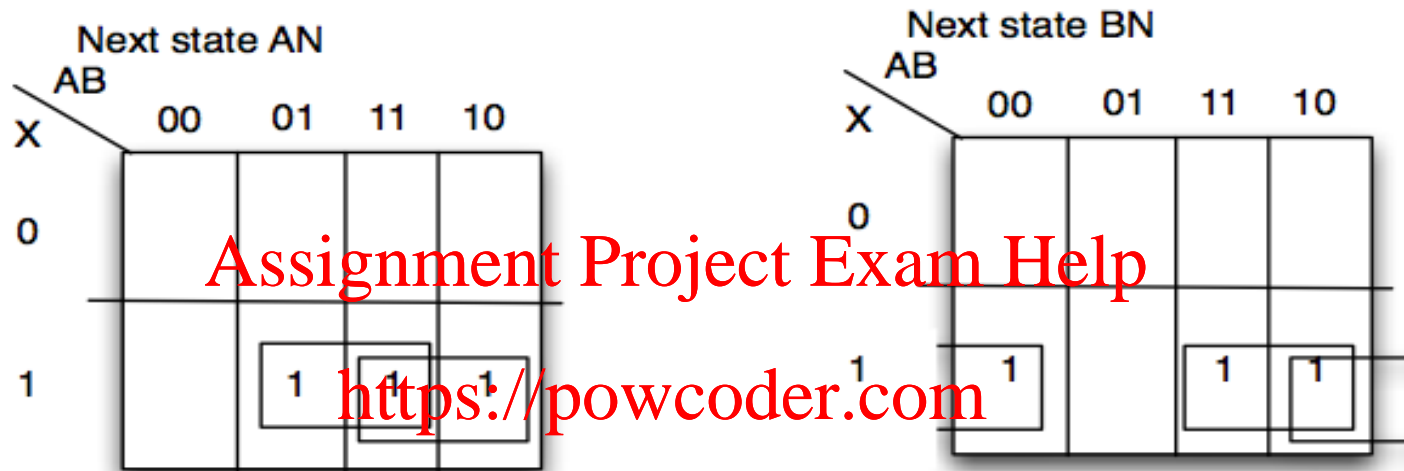

Add WeChat powcoder

$$A' = A X + B \bar{X} = (A + B) X$$

$$B' = A X + \bar{B} X = (A + \bar{B}) X$$

Truth Table for Output


AN	BN	Y
0	0	0
0	1	0
1	1	1
1	0	0

$$Y = AN \cdot BN$$

FSM Circuit

$$A' = A X + B X = (A + B) X$$
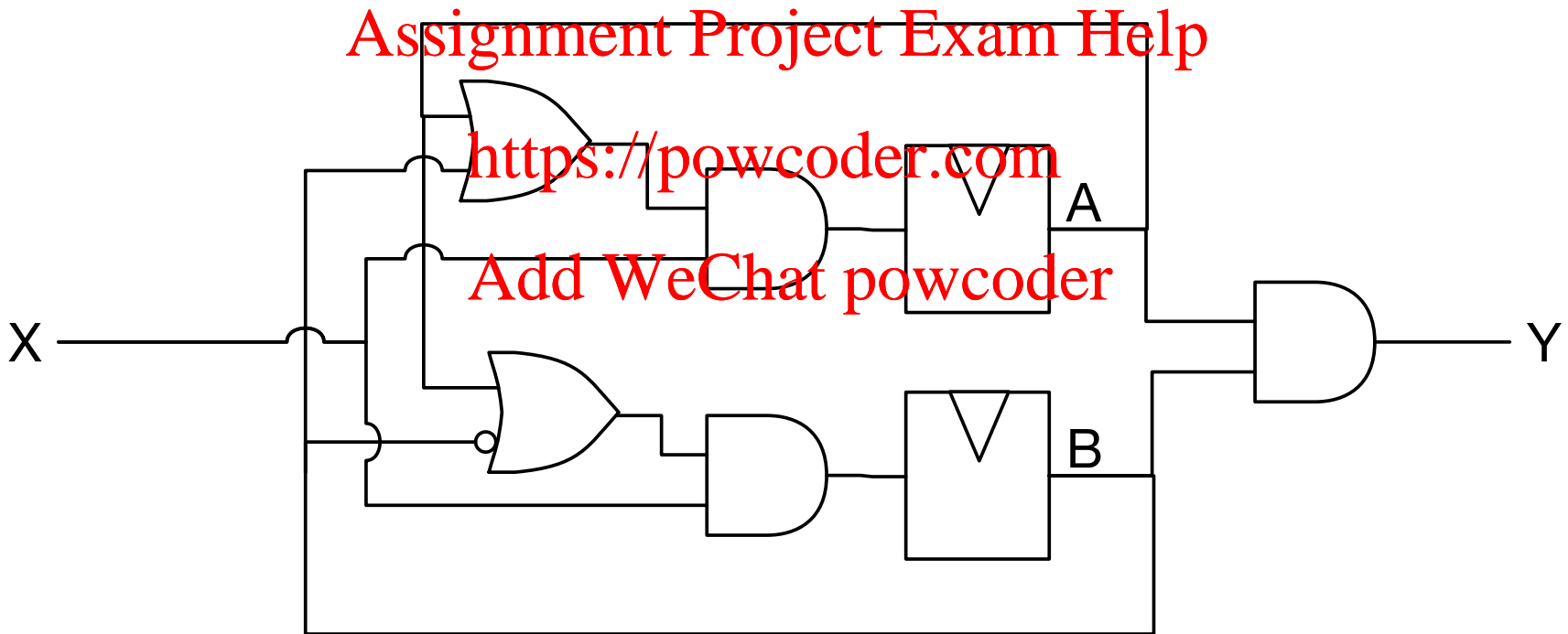
$$B' = A X + \overline{B} X = (A + \overline{B}) X$$



Backup

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


n-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type

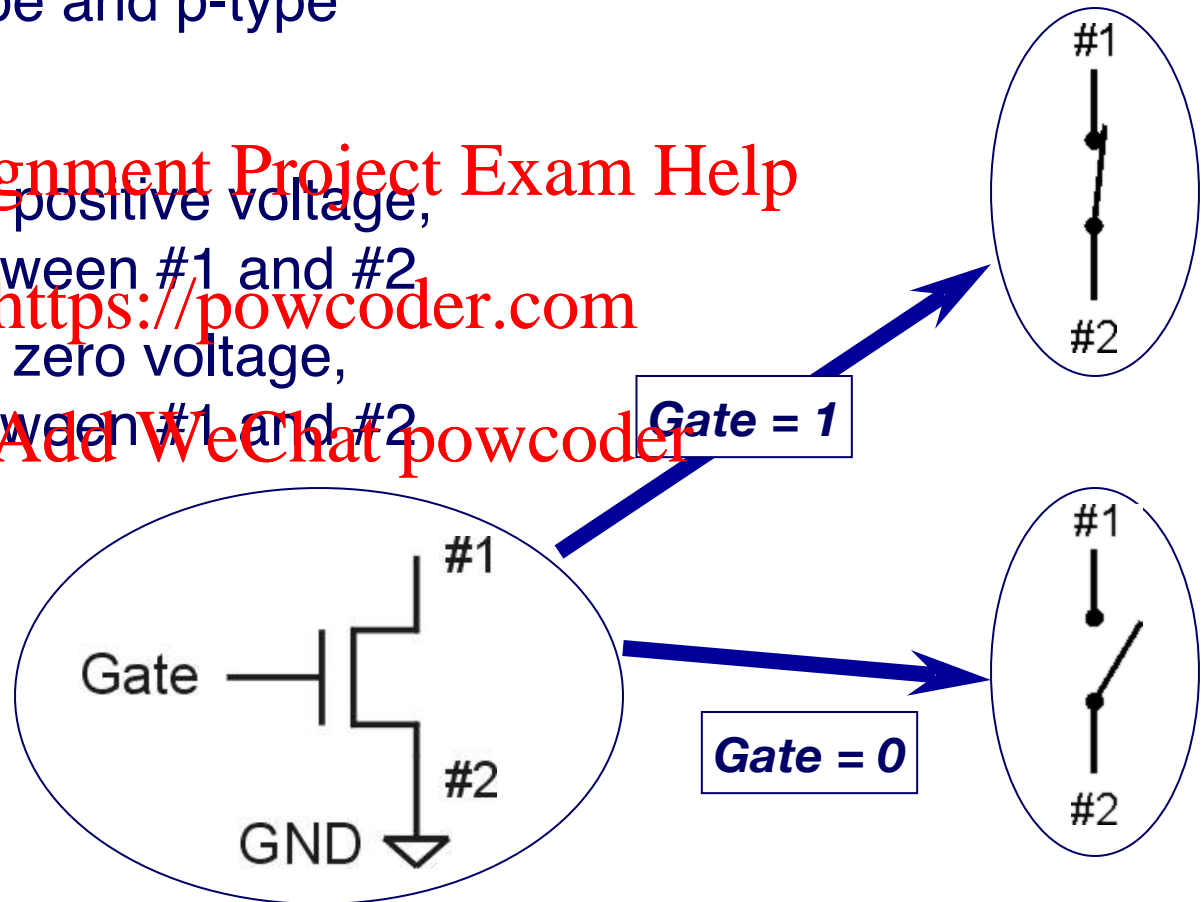- when Gate has positive voltage, short circuit between #1 and #2
- when Gate has zero voltage, open circuit between #1 and #2



p-type MOS Transistor


p-type is complementary to n-type

- when Gate has positive voltage, open circuit between #1 and #2
- when Gate has zero voltage, short circuit between #1 and #2

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

CMOS Circuit

Complementary MOS




Uses both n-type and p-type MOS transistors

- p-type
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
- n-type
 - Attached to GND
 - Pulls output voltage DOWN when input is one

MOS transistors are combined to form Logic Gates

For all inputs, make sure that output is either connected to GND or to +, but not both!

Inverter (NOT Gate)

   

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Truth table

In	Out
0 V	2.9 V
2.9 V	0 V

In	Out
0	1
1	0